

## Question 1

We know that  $V_p = 0.55V_s$  and  $V_n = 0.33V_s$

$$\begin{aligned}t_A &= RC \ln \left( \frac{V_P(V_S - V_n)}{V_n(V_S - V_p)} \right) \\&= 100\text{k}\Omega \cdot 10\mu\text{F} \cdot \ln \left( \frac{0.55(1 - 0.33)}{0.33(1 - 0.55)} \right) \\&= 0.9089\text{s}\end{aligned}$$

## Question 2

From the screen-shot, we see that the  $\Delta x$  is 0.892s. This is close to the calculated  $t_A$ . Therefore:

$$f_{\text{osc}} = \frac{1}{\Delta x} = 1.12\text{Hz}$$

## Question 3

We see that the period before

$$t_A = RC \ln \left( \frac{V_P(V_S - V_n)}{V_n(V_S - V_p)} \right)$$

and that the period now

$$t'_A = \frac{1}{2} RC \ln \left( \frac{V_P(V_S - V_n)}{V_n(V_S - V_p)} \right)$$

and therefore

$$t'_A = \frac{1}{2} t_A$$

the period is reduced by half (we should see the LED blinks faster)

## Question 4

The LED will blink super faster to an extent that the eye could not even capture the changes. The oscilloscope actually captured this change (as the screen-shot indicates).

## Question 5

The LED doesn't really affect the behavior of the circuit. The capacitor still discharge / charge in same amount of time no matter LED present or not. The LED, though, do play a role of visually indicating whether the circuit is in HIGH/LOW currently, and showing that the voltage is indeed, frequently changing between HIGH and LOW.

## Question 6

Submitted in team document.