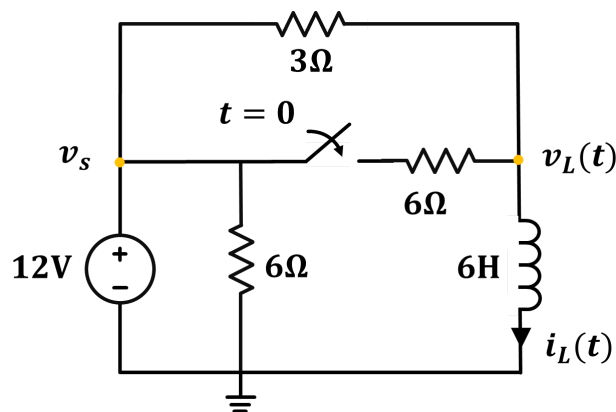


Problem 1

Sign acknowledging you will abide by this course's and the University's Academic Integrity policies or face sanctions for not doing so. These policies include, among others, plagiarism: representing the words or ideas of others as your own; cheating: using unauthorized materials and/or information. The possible sanctions include, among others, reduced letter grades and an F in the course. If your solution upload does not include your signature, your homework will NOT be graded, resulting in a zero.


Sign: Yuqing Zhai

Problem 2



(a)

Before the switch close, it looks like

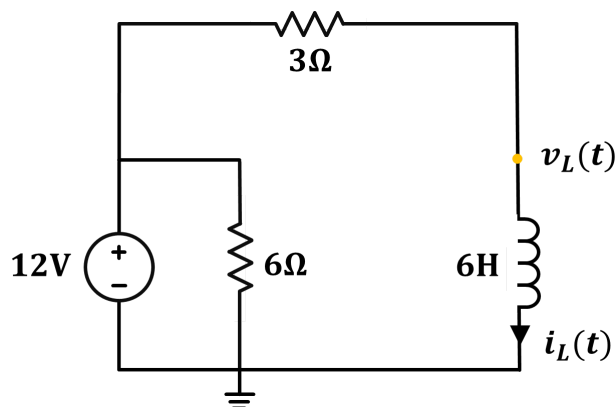

In the DC-steady state, the inductor will act like a short, therefore the voltage across it will be 0V. Using node-voltage method, we will see that

$$v_L(0^-) - 0V = 0V$$

which means that $v_L(0^-) = 0V$

Using node method, we see that

$$v_s - 0V = 12V$$

and therefore $v_s = 12V$. On node v_L , we see that


$$\frac{v_s - v_L(0^-)}{3\Omega} = i_L(0^-)$$

and therefore $i_L(0^-) = 4\text{A}$

(b)

See after (c)

(c)

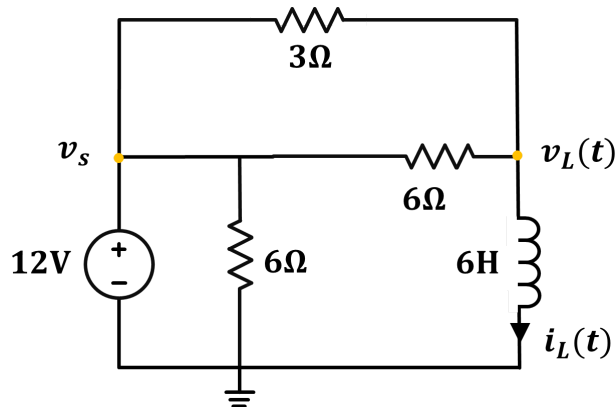

Using node voltage method on node $v_L(t)$

$$\frac{v_s - v_L(t)}{3} + \frac{v_s - v_L(t)}{6} = i_L(t)$$

$$\frac{v_s - v_L(t)}{2} = i_L(t)$$

We know that the inductor follows

$$v_L(t) = L \frac{di_L(t)}{dt}$$

Setting up the equation

$$v_s - v_L(t) = 2 \cdot i_L(t)$$

$$v_s - L \frac{di_L(t)}{dt} = 2 \cdot i_L(t)$$

$$v_s - 6 \cdot \frac{di_L(t)}{dt} = 2 \cdot i_L(t)$$

$$i_L'(t) + \frac{1}{3} \cdot i_L(t) = \frac{1}{3} \left(\frac{1}{2} v_s \right)$$

From the textbook 3.4.2, we know this form of equation has solution of

$$i_L(t) = (i_L(0^-) - \frac{1}{2} v_s) e^{-t/3} + \frac{1}{2} v_s$$

which is

$$i_L(t) = (4 - 6) e^{-t/3} + 6$$

$$\boxed{i_L(t) = (-2e^{-t/3} + 6)\text{A}}$$

and thus

$$\boxed{v_L(t) = L \frac{di_L(t)}{dt} = 6 \cdot -2 \cdot \left(-\frac{1}{3}\right) e^{-t/3} = (4e^{-t/3})\text{V}}$$

It's obvious that their $\tau = 3\text{s}$

(b)

From (c), we see that

$$i_L(t) = (i_L(0^-) - \frac{1}{2}v_s)e^{-t/3} + \frac{1}{2}v_s$$

$$i_L(t) = \frac{1}{2}v_s(1 - e^{-t/3}) + i_L(0^-)e^{-t/3}$$

$$\boxed{i_L(t) = (6(1 - e^{-t/3}) + 4e^{-t/3})\text{A}}$$

and we could see that

- Let $i_L(0^-) = 0$, the **zero-state response** is $\boxed{i_{L,ZS}(t) = \frac{1}{2}v_s(1 - e^{-t/3}) = 6(1 - e^{-t/3})}$
- Let $v_s = 0$, the **zero-input response** is $\boxed{i_{L,ZI} = i_L(0^-)e^{-t/3}} = 4e^{-t/3}\text{A}$


(d)




$$\tau = 3\text{s}$$

- The blue line is $v_L(t)$. At $t = 0^+$, $v_L = 4\text{V}$. As $t \rightarrow \infty$, $v_L \rightarrow 0\text{V}$. At $t = \tau$, $v_L(t) = 4e^{-1}\text{V}$
- The green line is $i_L(t)$. At $t = 0$, $i_L = 4\text{A}$. As $t \rightarrow \infty$, $v_L = 6\text{V}$. At $t = \tau$, $i_L(t) = (-2e^{-1} + 6)\text{A}$

Problem 3

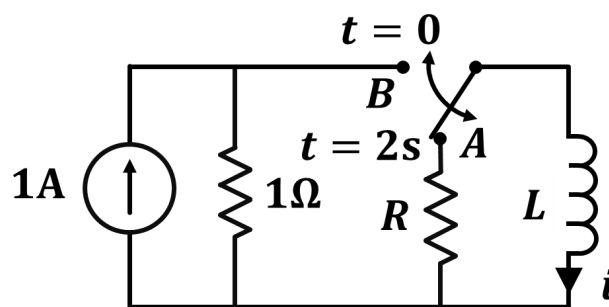

Before the $t = 0$:

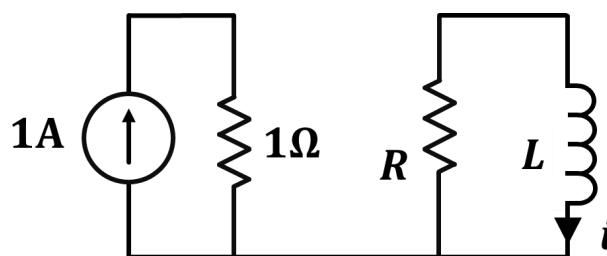

Since the switch has been in position A for a long time, the circuit will be in a steady state, and the inductor will act like a short.

Since in this case the 1Ω resistor will have 1A current (provided by the current source), using KCL on the node a , we see that


$$I + 1 = 1$$

that means the $I = 0\text{A}$, and therefore, do the KCL on the node b , we see the current on R is just i . Therefore, do the KVL as indicated, we see

$$Ri = v_L$$

since the inductor acts like a switch, $v_L = 0\text{V}$, and therefore $i(0) = 0\text{A}$

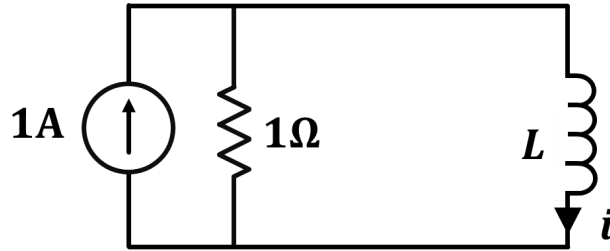At $t = 0$, when the switch moves to B , we see



From the textbook 3.4.2, this kind of circuit has the solution of

$$i(t) = (i(0^-) - I_s)e^{-\frac{t}{L/R}} + I_s$$

given $I_s = 1\text{A}$, $R = 1\Omega$ in this case, it is

$$i(t) = 1 - e^{-t/L}$$

at $t = 2\text{s}$, we want $i(2) = (1 - e^{-1})\text{A}$

$$i(2) = 1\text{A}(1 - e^{-2/L}) = (1 - e^{-1})\text{A}$$

$$-\frac{2}{L} = -1$$

$$\boxed{L = 2\text{H}}$$

Then after $t = 2\text{s}$, it moves back to A again, as mentioned earlier, that means

$$Ri(t) = v_L(t)$$

$$Ri(t) = L \frac{di(t)}{dt}$$

$$\frac{R}{L} dt = \frac{1}{i(t)} di(t)$$

$$\int_{2\text{s}}^t \frac{R}{L} ds = \int_{i(2\text{s})}^{i(t)} \frac{1}{i} di$$

$$\ln i(t) = \ln i(2) - \frac{R}{L}(t - 2)$$

$$i(t) = i(2)e^{-\frac{R}{L}(t-2)}$$

we know that $i(2) = (1 - e^{-1})\text{A}$. Therefore

$$i(t) = (1 - e^{-1})\text{A} \cdot e^{-\frac{R}{L}(t-2)}$$


we want $i(8) = (1 - e^{-1})e^{-2}\text{A}$, that is

$$i(8) = (1 - e^{-1})\text{A} \cdot e^{-\frac{R}{L}(8-2)} = (1 - e^{-1})e^{-2}\text{A}$$

$$-\frac{R}{L}(8-2) = -2$$

$$\boxed{R = \frac{L}{3} = \frac{2}{3}\Omega}$$

Problem 4

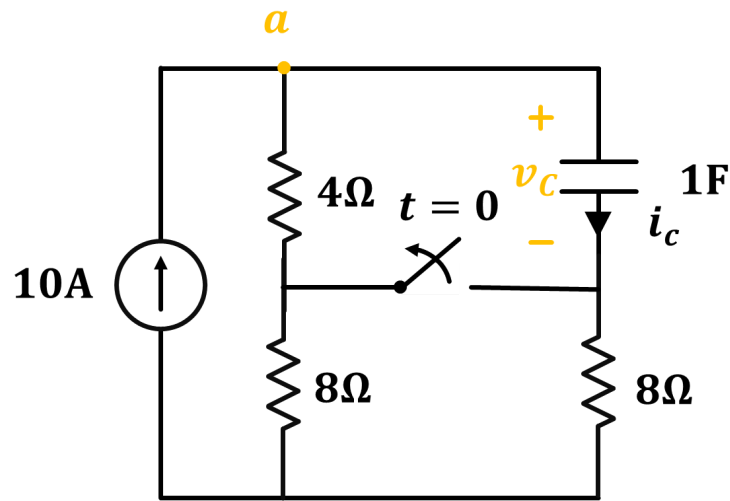

(a)

Since the switch has been closed for a long time, the capacitor will act like an open-circuit. Therefore

$i_C = 0\text{A}$ We see that in this case, the current flowing through the 4Ω is 10A . Therefore

$$\boxed{v_R(0^-) = 4\Omega \cdot 10\text{A} = 40\text{V}}$$

doing the KVL as indicated, we see that

$$\boxed{v_C(0^-) = v_R(0^-) = 40\text{V}}$$

(b)

See after (d)

(c)

Apply KCL at node a ,

$$i_s = i_R + i_C$$

and applying node-method at node a

$$v_a = i_R \cdot (4 + 8) = v_C + 8 \cdot i_C$$

At the capacitor

$$i_C = C \frac{dv_C}{dt} = 1 \frac{dv_C}{dt}$$

and therefore

$$12(i_s - i_C) = v_C + 8i_C$$

$$12i_s = 20i_C + v_C$$

$$20v'_C + v_C = 12i_s$$

$$v'_C + \frac{1}{20}v_C = \frac{1}{20}(12i_s)$$

From textbook 3.4.1, we know this kind of differential equation has solution

$$v_C(t) = (v_C(0^-) - 12i_s)e^{-t/20} + 12i_s$$

we know that $I_s = 10\text{A}$ and $v_C(0^-) = 40\text{V}$, therefore

$$v_C(t) = (-80e^{-t/20} + 120)\text{V}$$

therefore we know that

$$i_C = \frac{dv_C}{dt} = 4e^{-t/20}\text{A}$$

(d)

It follows that

$$i_R = i_s - i_c = (10 - 4e^{-t/20})\text{A}$$

and therefore

$$v_R = 4\Omega \cdot i_R = (40 - 16e^{-t/20})\text{V}$$

(b)

From (c), we see that

$$v_C(t) = (v_C(0^-) - 12i_s)e^{-t/20} + 12i_s$$


$$v_C(t) = 12i_s(1 - e^{-t/20}) + v_C(0^-)e^{-t/20}$$

$$v_C(t) = (120(1 - e^{-t/20}) + 40e^{-t/20})\text{V}$$

and we could see that

- Let $v_C(0^-) = 0$, the **zero-state response** is $v_{C,ZS}(t) = 12i_s(1 - e^{-t/20}) = 120(1 - e^{-t/20})\text{V}$
- Let $i_s = 0$, the **zero-input response** is $v_{C,ZI} = v_C(0^-)e^{-t/20} = 40e^{-t/20}\text{V}$

(e)

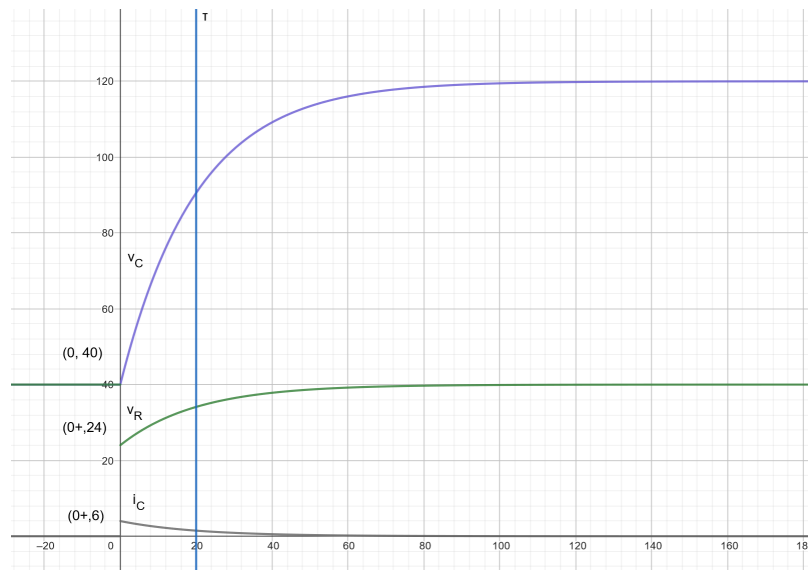


$\tau = 20\text{s}$

- The purple line is the $v_C(t)$. At $t = 0$, $v_C(t) = 40\text{V}$. As $t \rightarrow \infty$, $v_C(t) \rightarrow 120\text{V}$. At $t = \tau$, $v_C(t) = (-80e^{-1} + 120)\text{V}$

- The green line is the $v_R(t)$. At $t = 0^+$, $v_R(t) = 24\text{V}$. As $t \rightarrow \infty$, $v_R(t) = 40\text{V}$. At $t = \tau$, $v_R(t) = (40 - 16e^{-1})\text{V}$
- The gray line is the $i_C(t)$. At $t = 0^+$, $i_C(t) = 4\text{A}$. As $t \rightarrow \infty$, $i_C(t) = 0\text{A}$. At $t = \tau$, $i_C(t) = 4e^{-1}\text{A}$

Problem 5

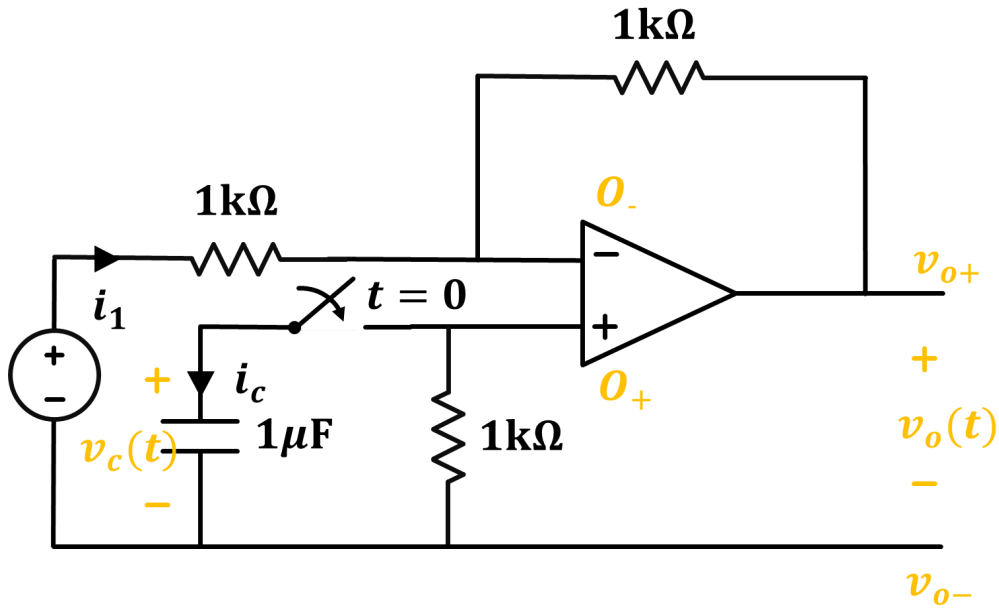

Using node-voltage method, we see that

$$v_{O+} - 0\text{V} = v_c(t)$$

therefore $v_{O+} = v_c(t)$, and therefore $v_{O-} = v_{O+} = v_c(t)$ under the ideal op-amp approximation. Therefore, the current i_1 is

$$i_1 = \frac{1\text{V} - v_c(t)}{1\text{k}\Omega}$$

since under ideal op-amp approximation

$$i_{O-} = i_{O+} = 0\text{A}$$

therefore at node O_- (using KCL)

$$\frac{v_c(t) - v_{o+}(t)}{1\text{k}\Omega} = \frac{1\text{V} - v_c(t)}{1\text{k}\Omega}$$

Notice the difference between v_{O+} and v_{o+}

and therefore we get

$$v_{o+}(t) = (2v_c(t) - 1)\text{V}$$

we see that at node O_+

$$\frac{v_c(t) - 0\text{V}}{1\text{k}\Omega} = -i_c(t)$$

and at the same time

$$i_c(t) = C \frac{dv_c(t)}{dt} = 1\mu\text{F} \cdot \frac{dv_c(t)}{dt}$$

therefore

$$v_c(t) = -1\text{k}\Omega \cdot 1\mu\text{F} \cdot \frac{dv_c(t)}{dt} = -1\text{mV} \cdot \text{s} \frac{dv_c}{dt}$$

and therefore (the derivation is similar to problem 3, so the process is skipped)

$$v_c(t) = v_c(0)e^{-1000t}\text{V}$$

therefore

$$v_{o+}(t) = (2v_c(0)e^{-1000t} - 1)\text{V}$$

Let $t = 2\text{ms}$, we get

$$\begin{aligned} v_{o+}(t) &= (2 \cdot (-2\text{V}) \cdot e^{-1000 \cdot 2\text{ms}} - 1)\text{V} \\ v_{o+}(t) &= (-4e^{-2} - 1)\text{V} \end{aligned}$$

we see that therefore

$$\boxed{v_o(t) = v_{o+}(t) - v_{o-}(t) = (-4e^{-2} - 1)\text{V} - 0\text{V} = (-4e^{-2} - 1)\text{V}}$$