

**Problem 1**

When there is light, the  $V_1$  will decrease and  $V_2$  will increase.  $V_1$  and  $V_2$  always add up to the voltage of the battery (roughly). The transistor roughly acts as a variable resistor since there is light, its resistance will increase (reflected as the increase in the  $V_2$ ).

**Problem 2**

$$V_2 = 0.06V, V_1 = 8.70V$$

$$\text{the } R_{DS}^{(\text{dark})} = \frac{0.06V}{8.70V} \cdot 1k\Omega = 0.00690k\Omega$$

**Problem 3**

$$V_2 = 8.55V, V_1 = 0.06V$$

$$\text{the } R_{DS}^{(\text{light})} = \frac{8.55V}{0.06V} \cdot 1k\Omega = 142.5k\Omega$$