

Problem 1


Sign acknowledging you will abide by this course's and the University's Academic Integrity policies or face sanctions for not doing so. These policies include, among others, plagiarism: representing the words or ideas of others as your own; cheating: using unauthorized materials and/or information. The possible sanctions include, among others, reduced letter grades and an F in the course. If your solution upload does not include your signature, your homework will NOT be graded, resulting in a zero.

Sign: Yuqing Zhai

Problem 2

For each one of the following two circuits, obtain R_{eq}


(a)

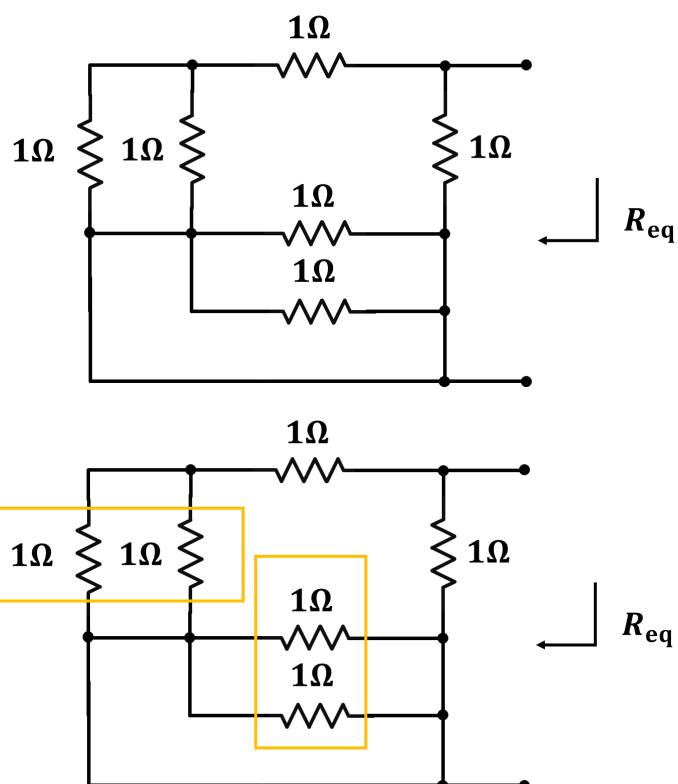


Apply the rule of **resistor in parallel**, the equivalent resistor for the section A and B , R_A and R_B respectively, is therefore

$$R_A = \frac{1\Omega \cdot 1\Omega}{1\Omega + 1\Omega} = \frac{1}{2}\Omega$$
$$R_B = \frac{1\Omega \cdot 1\Omega}{1\Omega + 1\Omega} = \frac{1}{2}\Omega$$

So we simplify the circuit:

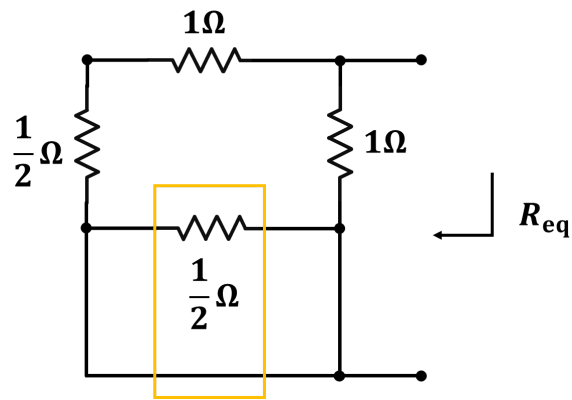

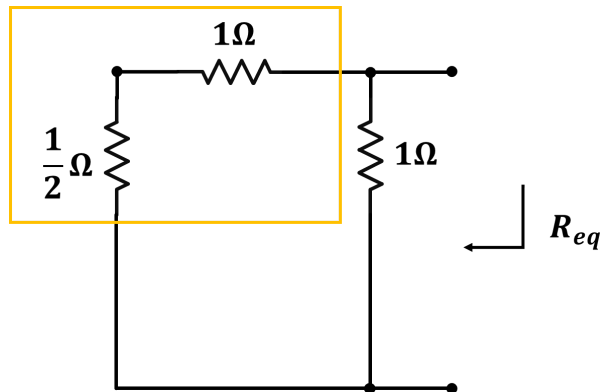
The resistor circled is in parallel with a wire, so it get short-circuited, and we could further simplify the circuit as:



Apply the rule of **resistor in series**, the equivalent resistor for that part is

$$R_{\text{equiv}} = 1\Omega + \frac{1}{2}\Omega = \frac{3}{2}\Omega$$

So we simplify the circuit:

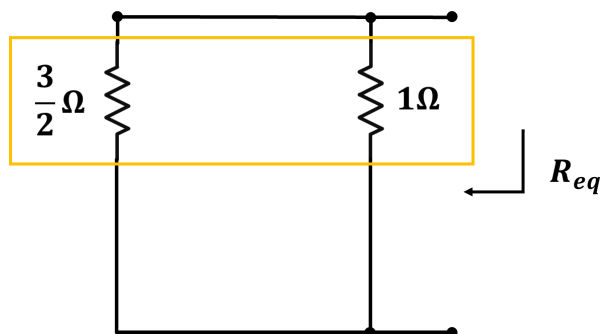


Apply the rule of **resistor in parallel** again, the equivalent resistor for that part is

$$R_{\text{eq}} = \frac{\frac{3}{2}\Omega \cdot 1\Omega}{\frac{3}{2}\Omega + 1\Omega} = \frac{3}{5}\Omega$$

So we simplify the circuit:



(b)

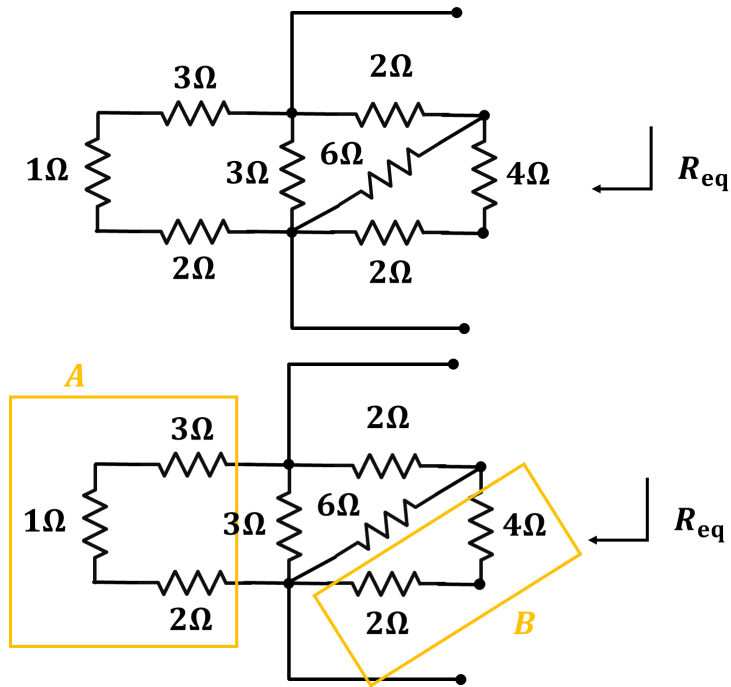


Apply the rule of **resistor in series**, the equivalent resistor for the section A and B , R_A and R_B respectively, is therefore

$$R_A = 1\Omega + 2\Omega + 3\Omega = 6\Omega$$

$$R_B = 2\Omega + 4\Omega = 6\Omega$$


So we simplify the circuit:

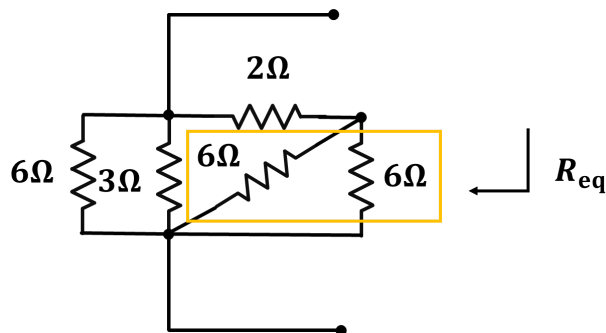

Apply the rule of **resistor in parallel**, the equivalent resistor for that part is

$$R_{\text{equiv}} = \frac{6\Omega \cdot 6\Omega}{6\Omega + 6\Omega} = 3\Omega$$


So we simplify the circuit:

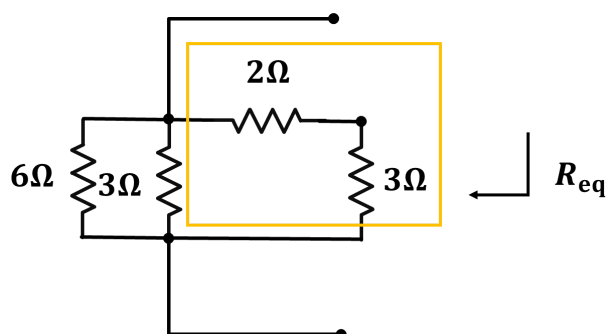

Apply the rule of **resistor in series**. the equivalent resistor for that part is

$$R_{\text{equiv}} = 2\Omega + 3\Omega = 5\Omega$$


So we simplify the circuit:

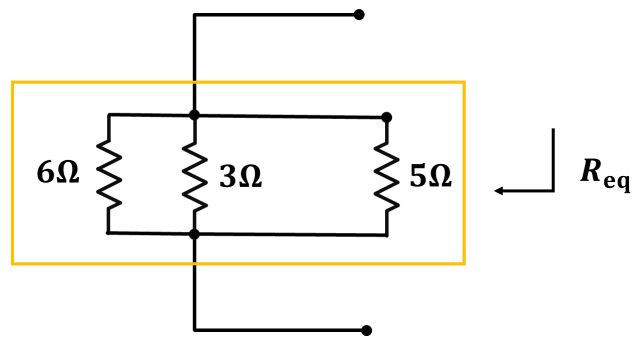

Apply the rule of **resistor in parallel**, the equivalent resistor for that part is



$$R_{eq} = \frac{1}{\frac{1}{6\Omega} + \frac{1}{3\Omega} + \frac{1}{5\Omega}} = \frac{10}{7}\Omega$$

So we simplify the circuit:

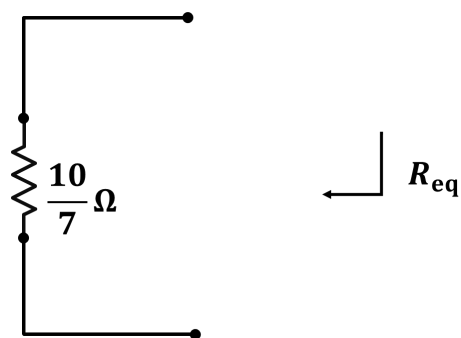

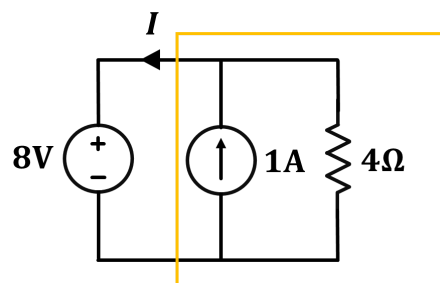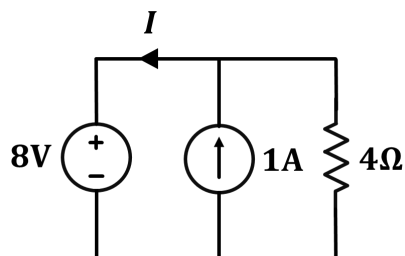Problem 3


Determine the current I in the following circuit using source transformation



Transform the selected region. We know that for a current source in parallel with a resistor, we could transform that into a voltage source in series with a resistor, where the I flows from $-$ to $+$ in the voltage source, and the voltage for that source is

$$V = 1A \cdot 4\Omega = 4V$$

Therefore we get:

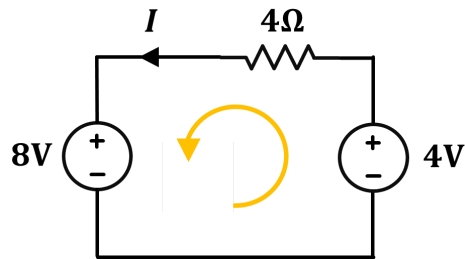


we could now apply KVL on the circuit and get

$$4\Omega \cdot I + 8V - 4V = 0$$

$$I = -\frac{4V}{4\Omega} = -1A$$

Problem 4

Consider the circuit below

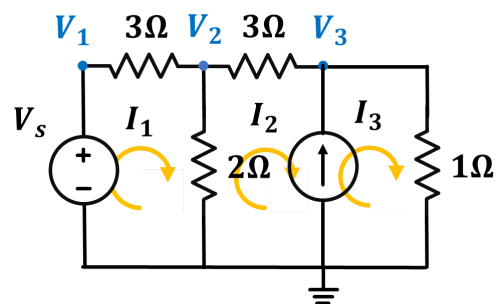

(a)

Use the loop-current method to obtain a set of three linearly independent equations, in terms of the loop currents I_1 , I_2 and I_3 , and the sources V_s and I_s , but no other variables, that can be used to determine the loop currents. Simplify your equations and write them with integer-valued coefficients.

On the left loop, we obtain (using KVL)

$$V_s = I_1 \cdot 3\Omega + (I_1 - I_2) \cdot 2\Omega$$

We also find

$$I_s = I_3 - I_2$$

On the outer loop, we obtain (using KVL)

$$V_s = I_1 \cdot 3\Omega + I_2 \cdot 3\Omega + I_3 \cdot 1\Omega$$

We could simplify these three equations.

$$V_s = I_1 \cdot 5\Omega - I_2 \cdot 2\Omega$$

$$I_s = I_3 - I_2$$

$$V_s = I_1 \cdot 3\Omega + I_2 \cdot 3\Omega + I_3 \cdot 1\Omega$$

and we get

$$\begin{aligned} I_1 &= \frac{3}{13\Omega} V_s - \frac{1}{13} I_s \\ I_2 &= \frac{1}{13\Omega} V_s - \frac{5}{26} I_s \\ I_3 &= \frac{1}{13\Omega} V_s + \frac{21}{26} I_s \end{aligned}$$

(b)

Use the node-voltage method to obtain a set of three

we see that on the node labeled V_2 , it has (using KCL)

$$\frac{V_1 - V_2}{3\Omega} = \frac{V_2 - 0}{2\Omega} + \frac{V_2 - V_3}{3\Omega}$$

we see that on the node labeled V_3 , it has (using KCL)

$$\frac{V_2 - V_3}{3\Omega} + I_s = \frac{V_3 - 0}{1\Omega}$$

We see that on the node labeled V_1 , we get

$$V_1 - 0 = V_s$$

and therefore, simply the equation

$$\begin{aligned} 2(V_1 - V_2) &= 3V_2 + 2(V_2 - V_3) \\ (V_2 - V_3) + 3\Omega \cdot I_s &= 3V_3 \\ V_1 &= V_s \end{aligned}$$


and

$$\begin{aligned} V_1 &= V_s \\ V_2 &= \frac{4}{13} V_s + \frac{3}{13} \Omega \cdot I_s \\ V_3 &= \frac{1}{13} V_s + \frac{21}{26} \Omega \cdot I_s \end{aligned}$$

(c)

It is known that $V_3 = k_1 V_s + k_2 I_s$. Use superposition to determine the values of k_1 and k_2 .

First remove the I_s .

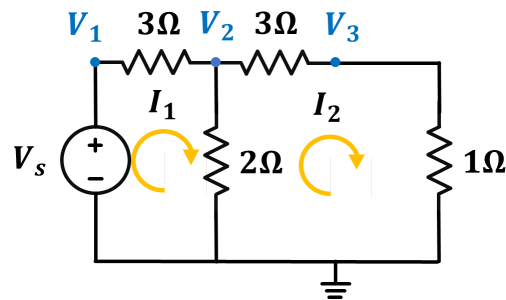

Use node voltage method, we see that on the node labeled V_2 , it has (using KCL)

$$\frac{V_1 - V_2}{3\Omega} = \frac{V_2 - 0}{2\Omega} + \frac{V_2 - V_3}{3\Omega}$$

and one the node labeled V_3 ,

$$\frac{V_2 - V_3}{3\Omega} = \frac{V_3 - 0}{1\Omega}$$

and we see that on the node labeled V_1 , we get

$$V_1 - 0 = V_s$$

So


$$2(V_1 - V_2) = 3V_2 + 2(V_2 - V_3)$$

$$(V_2 - V_3) = 3V_3$$

$$V_1 = V_s$$

We get $V_3 = \frac{1}{13}V_s$ which matches our value in (b).

Then, remove the V_s :

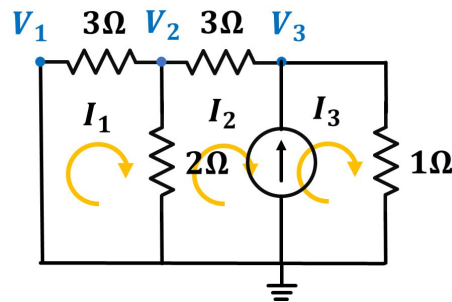

Use node-method, it basically follow the same procedure:

we see that on the node labeled V_2 , it has (using KCL)

$$\frac{V_1 - V_2}{3\Omega} = \frac{V_2 - 0}{2\Omega} + \frac{V_2 - V_3}{3\Omega}$$

we see that on the node labeled V_3 , it has (using KCL)

$$\frac{V_2 - V_3}{3\Omega} + I_s = \frac{V_3 - 0}{1\Omega}$$

We see that on the node labeled V_1 , we get

$$V_1 = 0$$

and therefore, simply the equation

$$-2V_2 = 3V_2 + 2(V_2 - V_3)$$

$$(V_2 - V_3) + 3\Omega \cdot I_s = 3V_3$$

$$V_1 = 0$$

and therefore we see that $V_3 = \frac{21}{26}I_s$, which matches our value in (b).

We therefore see that $k_1 = \frac{1}{13}$ and $k_2 = \frac{21}{26}$

(d)

Set $V_s = 10V$, and $I_s = 1A$. Therefore,

$$\begin{aligned}
 I_1 &= \frac{3}{13\Omega} 10\text{V} - \frac{1}{13} 1\text{A} = \frac{30}{13}\text{A} - \frac{1}{13}\text{A} = \frac{29}{13}\text{A} \\
 I_2 &= \frac{1}{13\Omega} 10\text{V} - \frac{5}{26} 1\text{A} = \frac{10}{13}\text{A} - \frac{5}{26}\text{A} = \frac{15}{26}\text{A} \\
 I_3 &= \frac{1}{13\Omega} 10\text{V} + \frac{21}{26} 1\text{A} = \frac{10}{13}\text{A} + \frac{21}{26}\text{A} = \frac{41}{26}\text{A}
 \end{aligned}$$


(e)

Set $V_s = 10\text{V}$, and $I_s = 1\text{A}$. Therefore,

$$\begin{aligned}
 V_1 &= V_s = 10\text{V} \\
 V_2 &= \frac{4}{13} 10\text{V} + \frac{3}{13} \Omega \cdot 1\text{A} = \frac{40}{13}\text{V} + \frac{3}{13}\text{V} = \frac{43}{13}\text{V} \\
 V_3 &= \frac{1}{13} 10\text{V} + \frac{21}{26} \Omega \cdot 1\text{A} = \frac{10}{13}\text{V} + \frac{21}{26}\text{V} = \frac{41}{26}\text{V}
 \end{aligned}$$

Problem 5

Consider the circuit below:

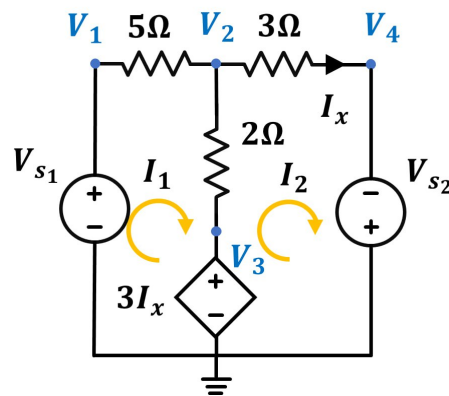

(a)

Use the loop-current method to obtain a set of linearly independent equations, in terms of the loop currents I_1 and I_2 , and the sources V_{s1} and V_{s2} , but no other variables, that can be used to determine the loop currents. Simplify your equations and write them with integer-valued coefficients.

On the left loop, we find (using KVL)

$$I_1 \cdot 5\Omega + (I_1 - I_2) \cdot 2\Omega + 3 \frac{\text{V}}{\text{A}} I_x = V_{s1}$$

On the right loop, we find

$$I_2 \cdot 3\Omega + (I_2 - I_1) \cdot 2\Omega = V_{s2} + 3 \frac{\text{V}}{\text{A}} I_x$$

we also know

$$I_2 = I_x$$

and therefore we find that

$$\begin{aligned}
 I_1 &= \frac{1}{8\Omega} \cdot V_{s1} - \frac{1}{16\Omega} \cdot V_{s2} \\
 I_2 &= \frac{1}{8\Omega} \cdot V_{s1} + \frac{7}{16\Omega} \cdot V_{s2}
 \end{aligned}$$

(b)

On the V_1 , we find

$$V_1 = V_{s_1}$$

and on the V_2 (using KCL), we find

$$\frac{V_1 - V_2}{5\Omega} = \frac{V_2 - V_3}{2\Omega} + I_x$$

and on the V_3 , we find that

$$V_3 = 3I_x$$

and on the V_4 , we find that

$$V_4 = -V_{s_2}$$


and we also know that

$$\frac{V_2 - V_4}{3\Omega} = I_x$$

therefore

$$\begin{aligned} V_1 &= V_{s_1} \\ V_2 &= \frac{3}{8}V_{s_1} + \frac{5}{16}V_{s_2} \\ V_3 &= \frac{3}{8}V_{s_1} + \frac{21}{16}V_{s_2} \\ V_4 &= -V_{s_2} \end{aligned}$$

(c)

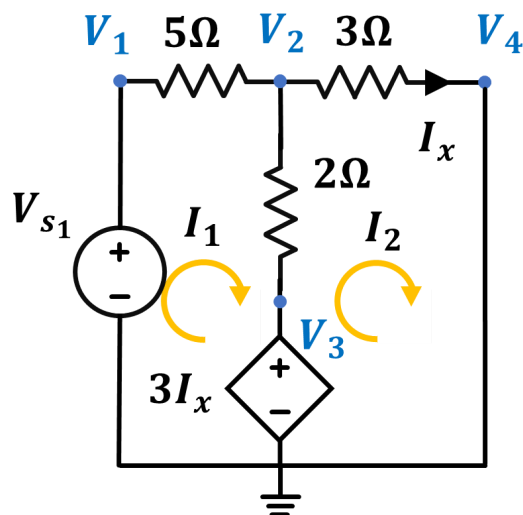

First remove V_{s_2} . Using node-voltage method, we see that

On the V_1 , we find

$$V_1 = V_{s_1}$$

and on the V_2 (using KCL), we find

$$\frac{V_1 - V_2}{5\Omega} = \frac{V_2 - V_3}{2\Omega} + I_x$$

and on the V_3 , we find that

$$V_3 = 3 \frac{\text{V}}{\text{A}} I_x$$

and on the V_4 , we find that

$$V_4 = 0\text{V}$$

and we also know that

$$\frac{V_2 - V_4}{3\Omega} = \frac{V_2 - 0\text{V}}{3\Omega} = I_x$$

therefore

$$V_1 = V_{s_1}$$


$$V_2 = \frac{3}{8} V_{s_1}$$

$$V_3 = \frac{3}{8} V_{s_1}$$

$$V_4 = 0\text{V}$$

we find $k_1 = \frac{3}{8}$

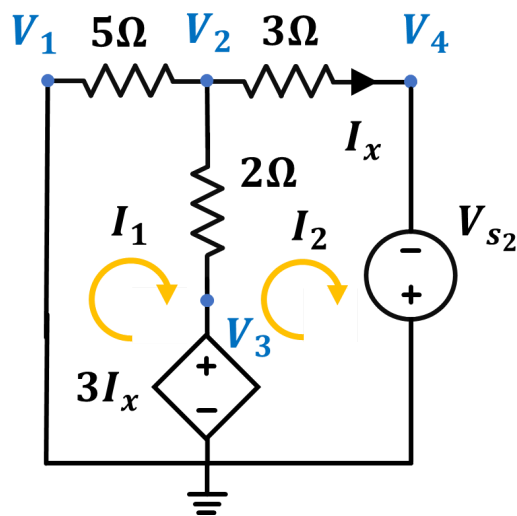Similarly, remove V_{s_1} . Using node-method again,



we find that

On the V_1 , we find

$$V_1 = 0$$

and on the V_2 (using KCL), we find

$$\frac{V_1 - V_2}{5\Omega} = \frac{V_2 - V_3}{2\Omega} + I_x$$

and on the V_3 , we find that

$$V_3 = 3I_x$$

and on the V_4 , we find that

$$V_4 = -V_{s_2}$$

and we also know that

$$\frac{V_2 - V_4}{3\Omega} = I_x$$

therefore

$$\begin{aligned}V_1 &= 0V \\V_2 &= \frac{5}{16}V_{s_2} \\V_3 &= \frac{21}{16}V_{s_2} \\V_4 &= -V_{s_2}\end{aligned}$$

we see that $k_2 = \frac{21}{16}$.

(d)

Set $V_{s_1} = 10V$ and $V_{s_2} = 4V$.

$$\begin{aligned}I_1 &= \frac{1}{8\Omega} \cdot 10V - \frac{1}{16\Omega} \cdot 4V = 1A \\I_2 &= \frac{1}{8\Omega} \cdot 10V + \frac{7}{16\Omega} \cdot 4V = 3A\end{aligned}$$

(e)

Set $V_{s_1} = 10V$ and $V_{s_2} = 4V$.

$$\begin{aligned}V_1 &= 10V \\V_2 &= \frac{3}{8} \cdot 10V + \frac{5}{16}4V = 5V \\V_3 &= \frac{3}{8} \cdot 10V + \frac{21}{16}4V = 9V \\V_4 &= -4V\end{aligned}$$