

## ECE 343 Lab #2: Diodes

### 1 Introduction

---

In this lab we'll be working with diodes and exploring some of their practical applications. The objectives for this lab are:

- Simulation of diode I-V curves.
- Using diodes as reference voltages
- Using diodes as a rectifier

### 2 Diodes-Review

---

In previous courses, you should have been introduced to diodes and simple models of their I-V behavior. We can create an ideal model of the diode that satisfies the following equations:

$$\begin{aligned} I_D &= 0 \text{ for } V \leq V_D \\ V &= V_D \text{ for } I_D \geq 0 \end{aligned}$$

This forms a “right-angle” curve on the current-versus-voltage  $v - i$  graph. While this is a nice approximation, real life models are not quite as simple. A key difference between the “ideal” diode you have seen earlier and a practical diode is that for a practical diode  $V \neq V_D$  when  $I_D \neq 0$ . The full semiconductor model of a diode is beyond the scope of this class. The  $v - i$  characteristic for a practical diode can be approximated using the following equation:

$$I_D = I_S(e^{V_D/V_T} - 1) \approx I_S e^{V_D/V_T}, \text{ if } V_D \gg V_T$$

where  $I_S$  is the reverse saturation current,  $I_D$  is the diode current,  $V_D$  is voltage across the diode terminals,  $V_T$  is a constant called thermal voltage. In figure 1 below, we plot an ideal model compared to a real one to show the difference.

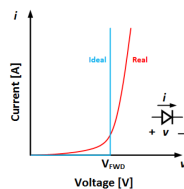


Figure 1: Ideal diode compared to real diode I-V curves.

### 3 Simulations

In this section we will perform *Spice* simulations to first obtain diode I – V characteristics and then explore how this diode can be used as a simple voltage reference.

#### 3.1 Diode Characterization


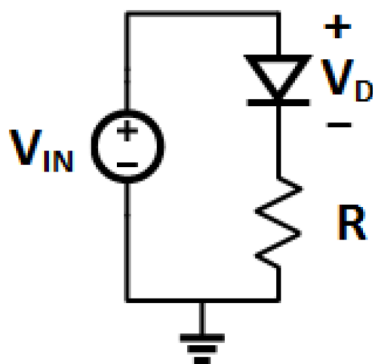


Figure 2: Diode characterization test bench

**Component Values:** Diode: 1N914/1N4148,  $V_{IN} = 4V$ ,  $R = 1k\Omega$

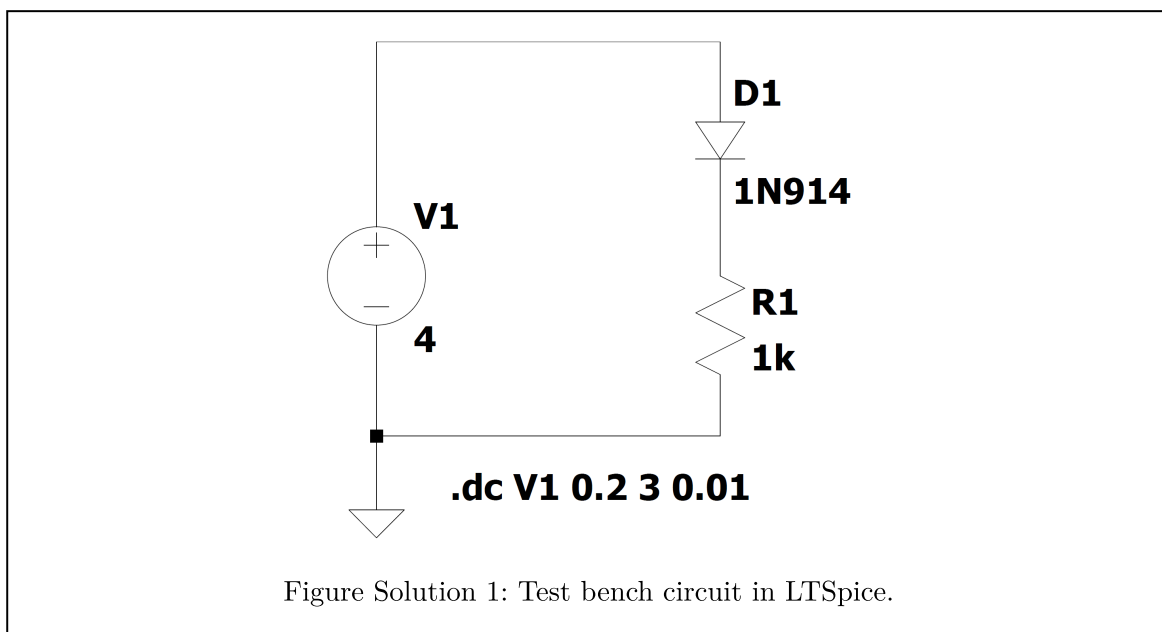1. Draw the circuit shown in Fig. 2 in LTSpice.




2. Perform a DC sweep simulation on the circuit. Use the following parameters:

- Source to sweep:  $V_{in}$
- Type of sweep: Linear

- Start Value: 0.2V
- Stop Value: 3V
- Increment: 0.01

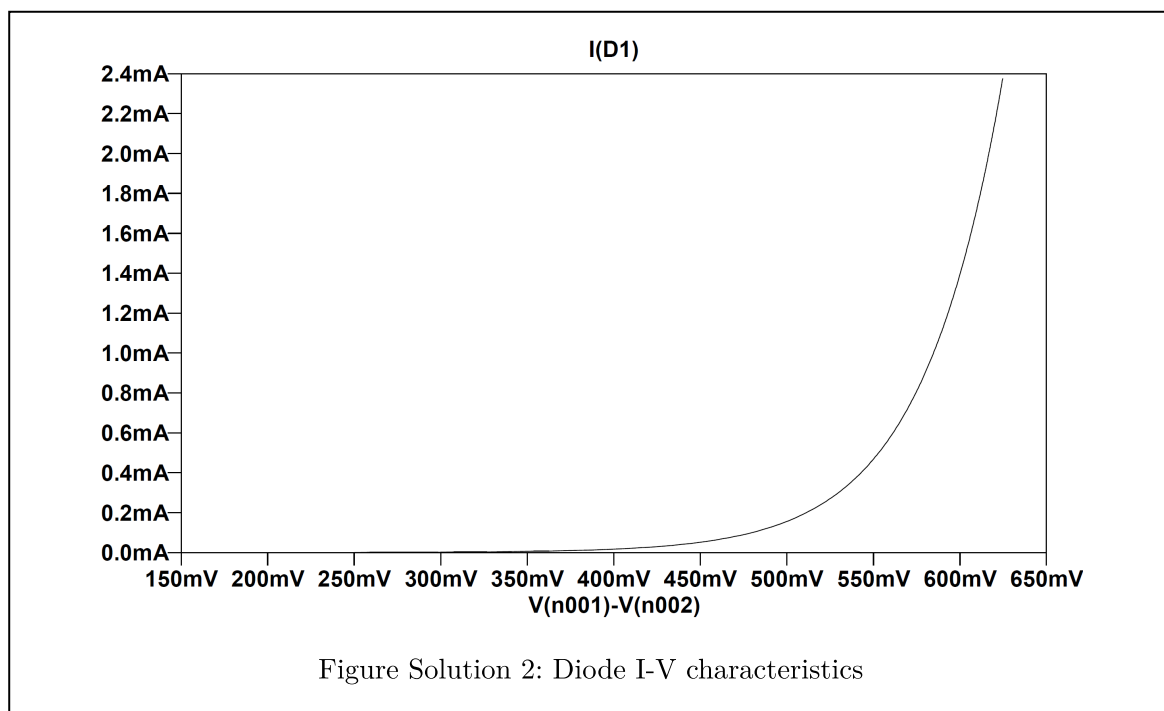3. Plot and take a screenshot of the I – V characteristics of the diode:

- The current can be selected by clicking directly on the diode.
- The voltage across the diode can be plotted by right-clicking the x-axis and typing in the correct formula in the “Quality Plotted” box.



4. What is  $V_{FWD}$  of the diode? (An approximate value of  $V_{FWD}$  can be found by extrapolating a line from the steepest part of the curve. To draw a line, right click the plot and select draw.)

$$V_{FWD} = 578.0\text{mV}$$

### 3.2 Diode as a Reference

When designing circuits, we often only have one voltage as an input:  $V_{DD}$ . With this in mind, we may also need different reference voltages and biases elsewhere in the circuit. One simple way to generate a reference voltage is by using a diode. In this section, we will explore how a diode can be used as a simple voltage reference.

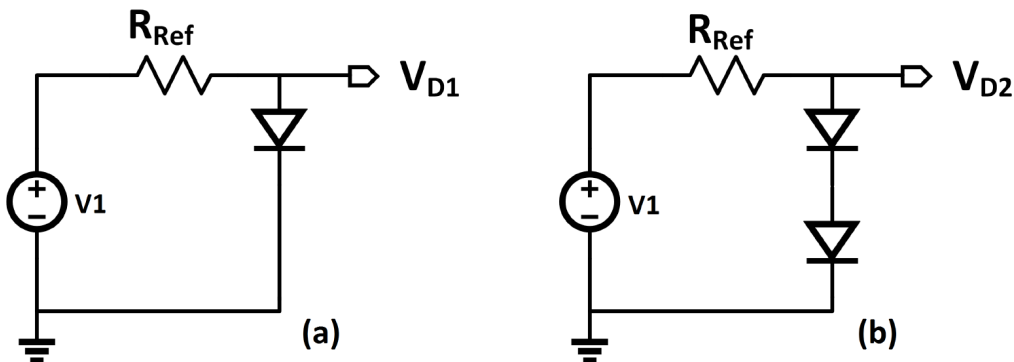


Figure 3: Left, one diode as a reference. Right two diodes as a reference.

1. Assuming we re using the same diodes in the previous section, compute the expected values of  $V_{D1}$ ,  $V_{D2}$ .

$$\begin{aligned} V_{D1} &= V_{FWD} = 578.0\text{mV} \\ V_{D2} &= 2 \cdot V_{FWD} = 2 \cdot 0.578\text{mV} = 1.156\text{V} \end{aligned}$$


2. Now assume that the source voltage has a sinusoidal noise component (i.e.  $V_1 = V_{DC} + v_n \sin(2\pi \cdot 100t)$ ). Derive an expression for the incremental output voltage ( $\Delta V_0$ ) in terms of the diode incremental resistance  $r_d$  for **each** circuit.

The diode is essentially a resistor with resistance  $r_d$  in incremental analysis. So,


$$\begin{aligned} \Delta V_{01} &= \frac{r_d}{r_d + R_{ref}} v_n; \\ \Delta V_{02} &= \frac{2 \cdot r_d}{2 \cdot r_d + R_{ref}} v_n \end{aligned}$$

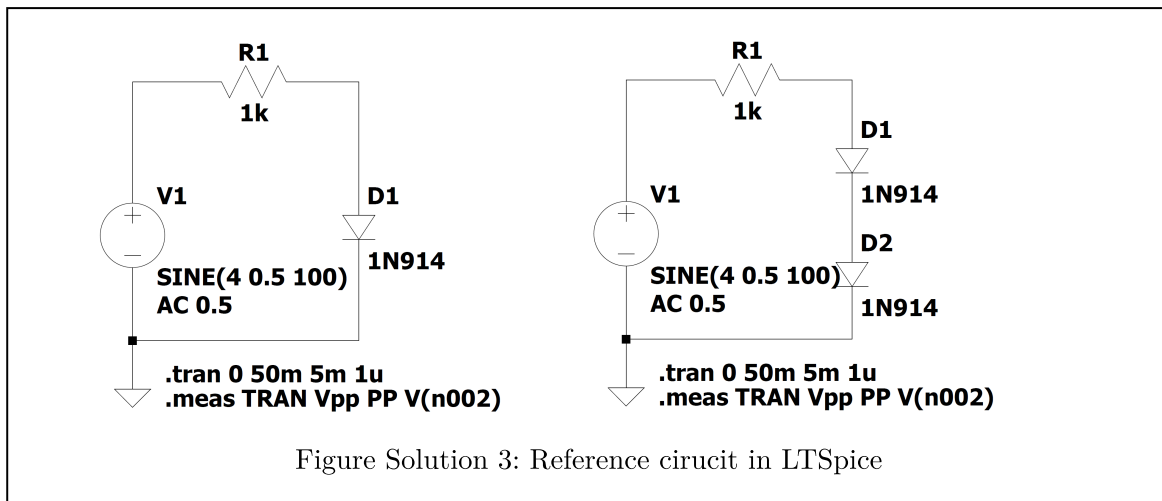3. Draw the circuits shown in Fig. 3 in LTspice. Let  $V_1 = 4 + 0.5 \sin(2\pi \cdot 100t)\text{V}$  and  $R_{ref} = 1\text{k}\Omega$ . Make sure to use the 1N914 diodes as before. Perform a **transient** simulation on the circuits with the following parameters:

- Stop time: 50m
- Time to start saving data: 5m
- Maximum timestep: 1u



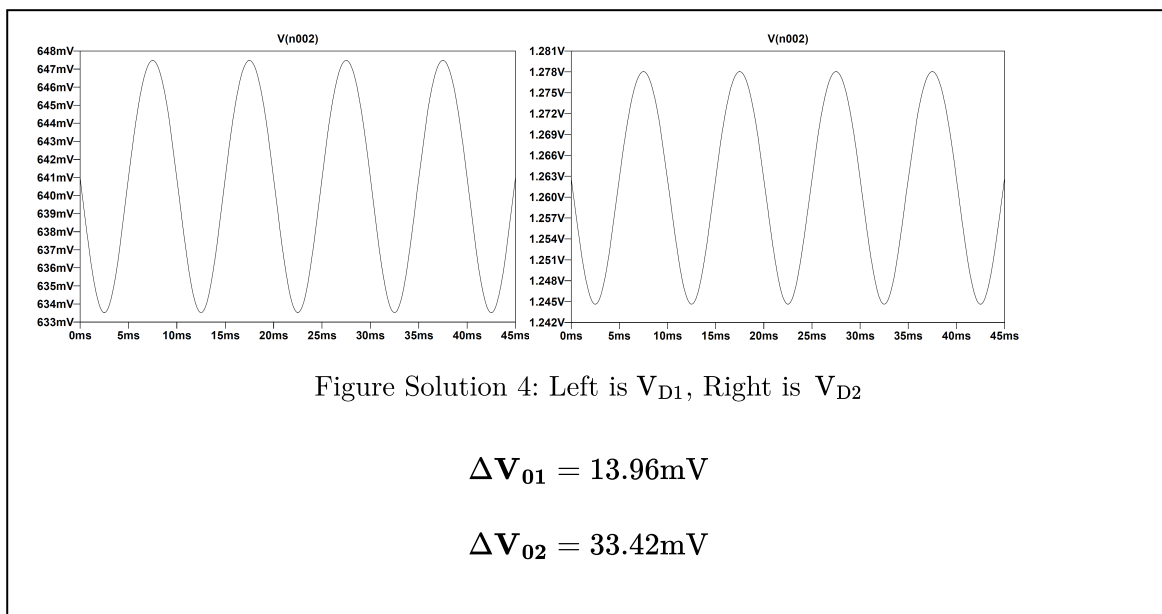4. Note down the peak-to-peak variation in output voltage ( $\Delta V_0$ ) for both circuits. Take a screenshot of one of the plots.



### 3.3 Diode Reference Test Circuit

In an ideal reference, the output voltage should not change under any load conditions. We will now see how well the diode based reference circuit discussed in section 3.1 acts under different load conditions.


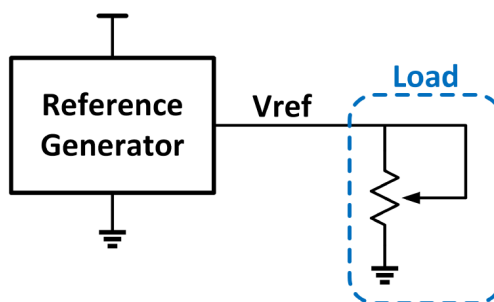


Figure 4: Simple reference generator measurement circuit

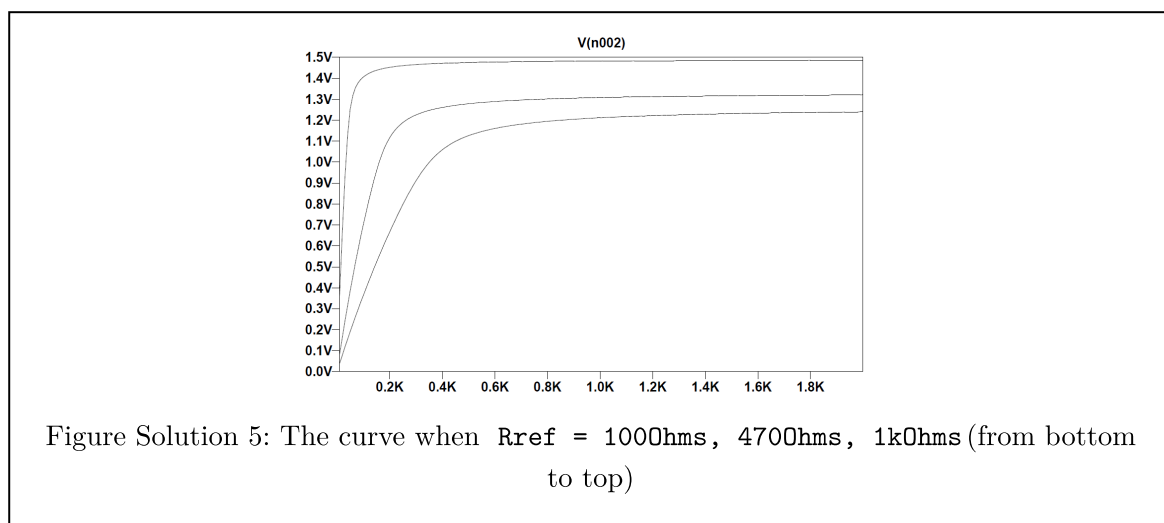1. Draw the voltage reference circuit shown in 3(b) with a resistive load  $R_L$  as shown in Fig. 4. Set  $V_1 = 4 + 0.5 \sin(2\pi \cdot 100t)$  with  $R_{ref} = 100\Omega$ . Perform a **DC operating point** simulation while sweeping the resistive load from  $10\Omega$  to  $2k\Omega$  with an increment of  $10\Omega$ . Please refer to the LTSpice tutorial on the website for details on how to set the resistor as the sweep variable.
2. In LTSpice, plot  $V_{ref}$  vs  $R_L$  and record the  $R_L$  at which the curve is 95% of the maximum voltage (use your best estimation in getting  $R_{L, min}$ ). Take a screenshot of your graph.
3. Repeat steps 1 and 2 for  $R_{ref} = 470\Omega$  and  $R_{ref} = 1k\Omega$ ,



4. Use  $R_{ref} = 100\Omega$  and replace the load resistor with its corresponding  $R_{L, min}$ .

5. Run a transient simulation and record the value of  $\Delta V_0$ ,  $P_{\text{supplied}}$ , and  $P_{\text{load}}$  in Table 1 (**HINT**: Instantaneous  $P_{\text{supplied}}$  and  $P_{\text{load}}$  can be obtained by holding the “alt” key and clicking on the component to be measured. Average power can be obtained by holding “ctrl” button and clicking on the name of the measurement in the waveform window.
6. Repeat steps 4 and 5 for  $R_{\text{ref}} = 470\Omega$  and  $R_{\text{ref}} = 1k\Omega$ .

Table 1: Performance of a Diode based Voltage Regulator

$R_{\text{ref}}$	$\Delta V_0$	$P_{\text{supplied}}$	$P_{\text{load}}$	$R_{L,\text{min}}$
$100\Omega$	72.96mV	-103.38mW	18.21mW	$110\Omega$
$470\Omega$	68.66mV	-23.35mW	4.148mW	$380\Omega$
$1k\Omega$	71.81mV	-11.29mW	2.039mW	$680\Omega$

7. From the table above, briefly explain what happens as a larger  $R_{\text{ref}}$  is used.

When a larger  $R_{\text{ref}}$  is used, the  $P_{\text{supplied}}$ , and  $P_{\text{load}}$  decreases (since current is limited, of course.), and the  $R_{L,\text{min}}$  increases. The  $\Delta V_0$  doesn't seem to change, it always around 70mV.