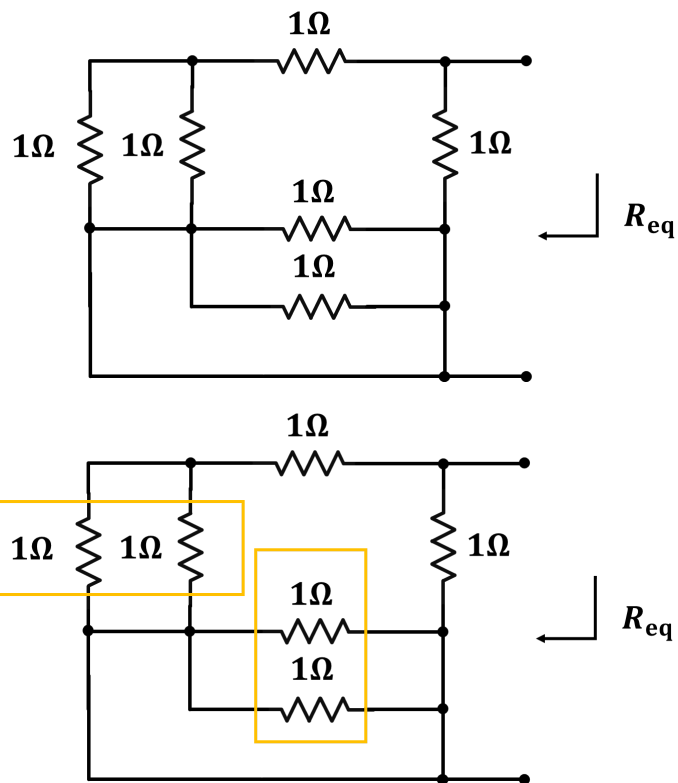


## Problem 2

For each one of the following two circuits, obtain  $R_{eq}$

(a)




Apply the rule of **resistor in parallel**, the equivalent resistor for the section  $A$  and  $B$ ,  $R_A$  and  $R_B$  respectively, is therefore


$$R_A = \frac{1\Omega \cdot 1\Omega}{1\Omega + 1\Omega} = \frac{1}{2}\Omega$$

$$R_B = \frac{1\Omega \cdot 1\Omega}{1\Omega + 1\Omega} = \frac{1}{2}\Omega$$

So we simplify the circuit:

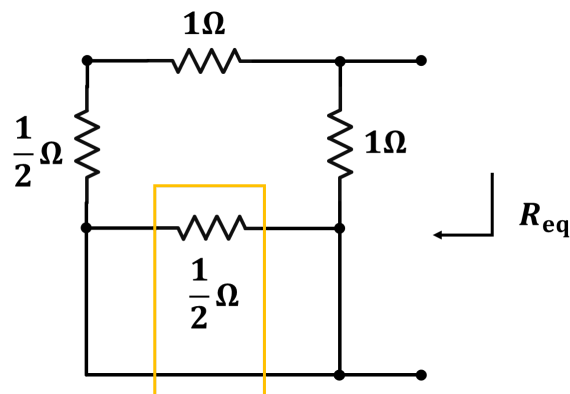

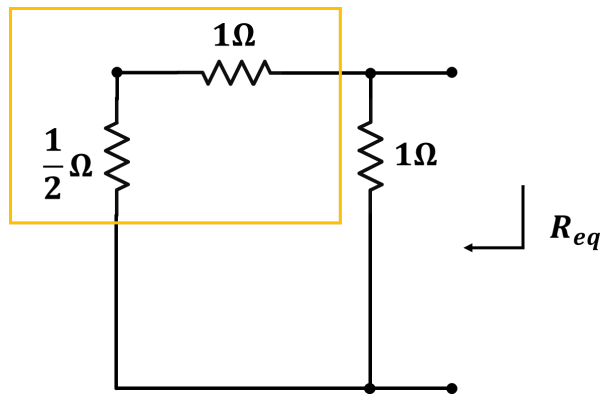
The resistor circled is in parallel with a wire, so it get short-circuited, and we could further simplify the circuit as:



Apply the rule of **resistor in series**, the equivalent resistor for that part is

$$R_{eqiv} = 1\Omega + \frac{1}{2}\Omega = \frac{3}{2}\Omega$$

So we simplify the circuit:

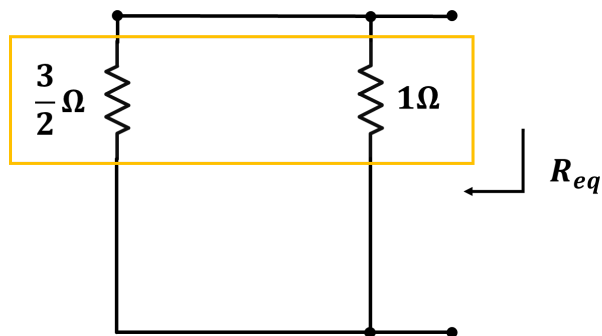


Apply the rule of **resistor in parallel** again, the equivalent resistor for that part is


$$R_{eq} = \frac{\frac{3}{2}\Omega \cdot 1\Omega}{\frac{3}{2}\Omega + 1\Omega} = \frac{3}{5}\Omega$$

So we simplify the circuit:



(b)

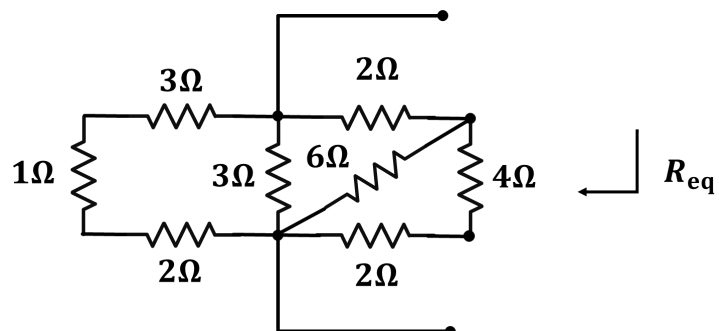

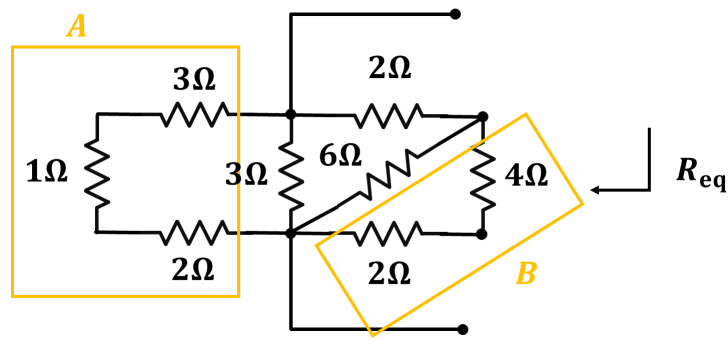


Apply the rule of **resistor in series**, the equivalent resistor for the section  $A$  and  $B$ ,  $R_A$  and  $R_B$  respectively, is therefore

$$R_A = 1\Omega + 2\Omega + 3\Omega = 6\Omega$$

$$R_B = 2\Omega + 4\Omega = 6\Omega$$


So we simplify the circuit:

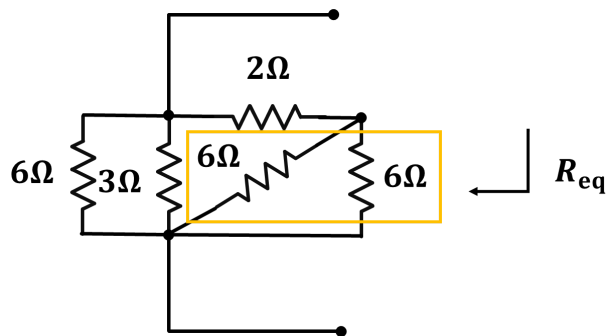

Apply the rule of **resistor in parallel**, the equivalent resistor for that part is

$$R_{equiv} = \frac{6\Omega \cdot 6\Omega}{6\Omega + 6\Omega} = 3\Omega$$


So we simplify the circuit:

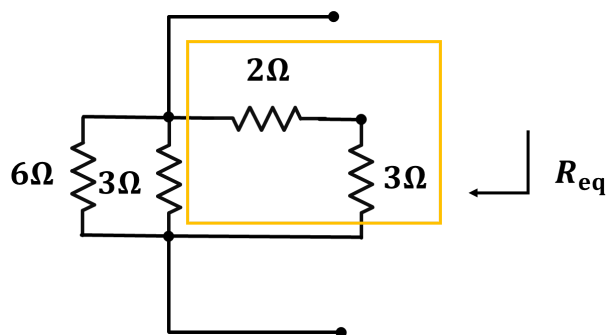

Apply the rule of **resistor in series**. the equivalent resistor for that part is

$$R_{equiv} = 2\Omega + 3\Omega = 5\Omega$$


So we simplify the circuit:

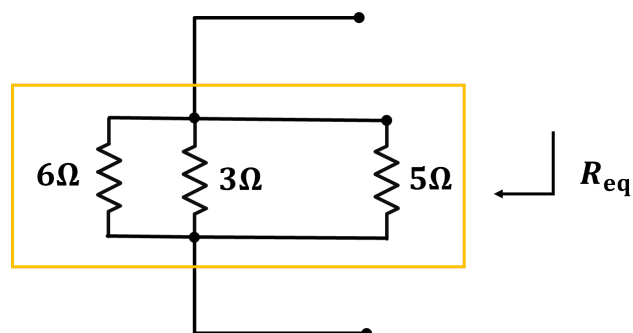

Apply the rule of **resistor in parallel**, the equivalent resistor for that part is


$$R_{eq} = \frac{1}{\frac{1}{6\Omega} + \frac{1}{3\Omega} + \frac{1}{5\Omega}} = \frac{10}{7}\Omega$$

So we simplify the circuit:

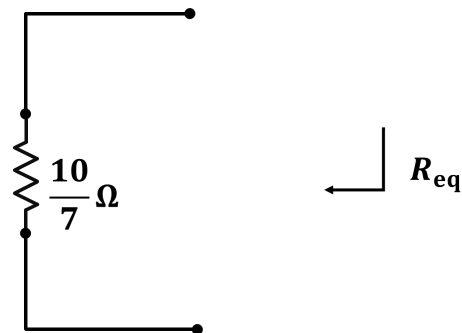
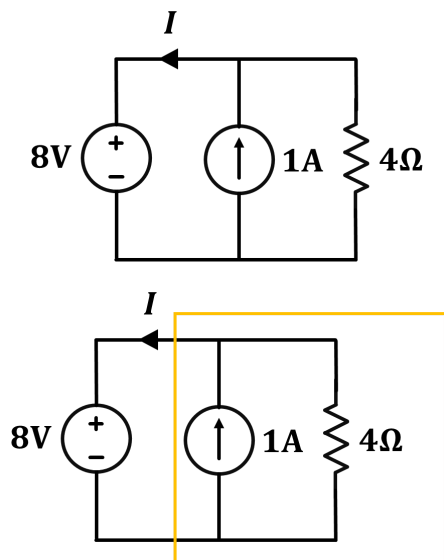
### Problem 3


Determine the current  $I$  in the following circuit using source transformation



Transform the selected region. We know that for a current source in parallel with a resistor, we could transform that into a voltage source in series with a resistor, where the  $I$  flows from  $-$  to  $+$  in the voltage source, and the voltage for that source is

$$V = 1A \cdot 4\Omega = 4V$$

Therefore we get:

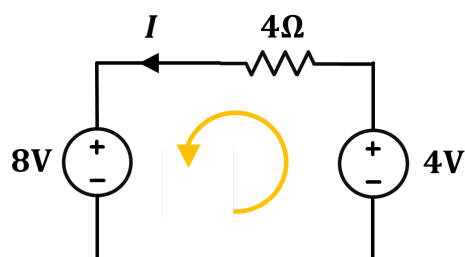


we could now apply KVL on the circuit and get

$$4\Omega \cdot I + 8V - 4V = 0$$

$$I = -\frac{4V}{4\Omega} = -1A$$

## Problem 4

Consider the circuit below

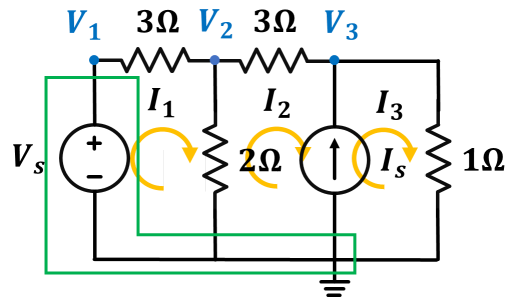

(a)

Use the loop-current method to obtain a set of three linearly independent equations, in terms of the loop currents  $I_1$ ,  $I_2$  and  $I_3$ , and the sources  $V_s$  and  $I_s$ , but no other variables, that can be used to determine the loop currents. Simplify your equations and write them with integer-valued coefficients.

On the left loop, we obtain (using KVL)

$$V_s = I_1 \cdot 3\Omega + (I_1 - I_2) \cdot 2\Omega$$

We also find

$$I_s = I_3 - I_2$$

On the outer loop, we obtain (using KVL)

$$V_s = I_1 \cdot 3\Omega + I_2 \cdot 3\Omega + I_3 \cdot 1\Omega$$

We could simplify these three equations.

$$\begin{aligned} V_s &= I_1 \cdot 5\Omega - I_2 \cdot 2\Omega \\ I_s &= I_3 - I_2 \\ V_s &= I_1 \cdot 3\Omega + I_2 \cdot 3\Omega + I_3 \cdot 1\Omega \end{aligned}$$

and we get

$$\begin{cases} I_1 = \frac{3}{13\Omega} V_s - \frac{1}{13} I_s \\ I_2 = \frac{1}{13\Omega} V_s - \frac{5}{26} I_s \\ I_3 = \frac{1}{13\Omega} V_s + \frac{21}{26} I_s \end{cases}$$

(b)

Use the node-voltage method to obtain a set of three

we see that on the node labeled  $V_2$ , it has (using KCL)

$$\frac{V_1 - V_2}{3\Omega} = \frac{V_2 - 0}{2\Omega} + \frac{V_2 - V_3}{3\Omega}$$

we see that on the node labeled  $V_3$ , it has (using KCL)

$$\frac{V_2 - V_3}{3\Omega} + I_s = \frac{V_3 - 0}{1\Omega}$$

We see that on the node labeled  $V_1$ , we get

$$V_1 - 0 = V_s$$

and therefore, simply the equation

$$\begin{aligned} 2(V_1 - V_2) &= 3V_2 + 2(V_2 - V_3) \\ (V_2 - V_3) + 3\Omega \cdot I_s &= 3V_3 \\ V_1 &= V_s \end{aligned}$$


and

$$\begin{aligned} V_1 &= V_s \\ V_2 &= \frac{4}{13}V_s + \frac{3}{13}\Omega \cdot I_s \\ V_3 &= \frac{1}{13}V_s + \frac{21}{26}\Omega \cdot I_s \end{aligned}$$

(c)

It is known that  $V_3 = k_1 V_s + k_2 I_s$ . Use superposition to determine the values of  $k_1$  and  $k_2$ .

First remove the  $I_s$ .

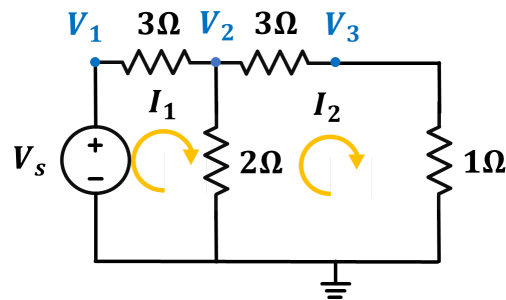

Use node voltage method, we see that on the node labeled  $V_2$ , it has (using KCL)

$$\frac{V_1 - V_2}{3\Omega} = \frac{V_2 - 0}{2\Omega} + \frac{V_2 - V_3}{3\Omega}$$

and on the node labeled  $V_3$ ,

$$\frac{V_2 - V_3}{3\Omega} = \frac{V_3 - 0}{1\Omega}$$

and we see that on the node labeled  $V_1$ , we get


$$V_1 - 0 = V_s$$

So

$$\begin{aligned} 2(V_1 - V_2) &= 3V_2 + 2(V_2 - V_3) \\ (V_2 - V_3) &= 3V_3 \\ V_1 &= V_s \end{aligned}$$

We get  $V_3 = \frac{1}{13}V_s$  which matches our value in (b).

Then, remove the  $V_s$ :

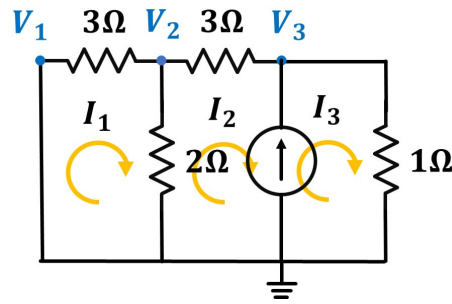

Use node-method, it basically follow the same procedure:

we see that on the node labeled  $V_2$ , it has (using KCL)

$$\frac{V_1 - V_2}{3\Omega} = \frac{V_2 - 0}{2\Omega} + \frac{V_2 - V_3}{3\Omega}$$

we see that on the node labeled  $V_3$ , it has (using KCL)

$$\frac{V_2 - V_3}{3\Omega} + I_s = \frac{V_3 - 0}{1\Omega}$$

We see that on the node labeled  $V_1$ , we get

$$V_1 = 0$$

and therefore, simply the equation

$$\begin{aligned} -2V_2 &= 3V_2 + 2(V_2 - V_3) \\ (V_2 - V_3) + 3\Omega \cdot I_s &= 3V_3 \\ V_1 &= 0 \end{aligned}$$

and therefore we see that  $V_3 = \frac{21}{26} I_s$ , which matches our value in (b).

We therefore see that  $k_1 = \frac{1}{13}$  and  $k_2 = \frac{21}{26}$

(d)

Set  $V_s = 10V$ , and  $I_s = 1A$ . Therefore,

$$\begin{aligned} I_1 &= \frac{3}{13\Omega} 10V - \frac{1}{13} 1A = \frac{30}{13} A - \frac{1}{13} A = \frac{29}{13} A \\ I_2 &= \frac{1}{13\Omega} 10V - \frac{5}{26} 1A = \frac{10}{13} A - \frac{5}{26} A = \frac{15}{26} A \\ I_3 &= \frac{1}{13\Omega} 10V + \frac{21}{26} 1A = \frac{10}{13} A + \frac{21}{26} A = \frac{41}{26} A \end{aligned}$$


(e)

Set  $V_s = 10V$ , and  $I_s = 1A$ . Therefore,

$$\begin{aligned} V_1 &= V_s = 10V \\ V_2 &= \frac{4}{13} 10V + \frac{3}{13} \Omega \cdot 1A = \frac{40}{13} V + \frac{3}{13} V = \frac{43}{13} V \\ V_3 &= \frac{1}{13} 10V + \frac{21}{26} \Omega \cdot 1A = \frac{10}{13} V + \frac{21}{26} V = \frac{41}{26} V \end{aligned}$$

## Problem 5

Consider the circuit below:

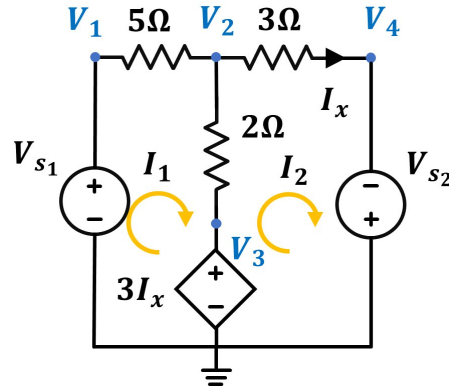

(a)

Use the loop-current method to obtain a set of linearly independent equations, in terms of the loop currents  $I_1$  and  $I_2$ , and the sources  $V_{s1}$  and  $V_{s2}$ , but no other variables, that can be used to determine the loop currents. Simplify your equations and write them with integer-valued coefficients.

On the left loop, we find (using KVL)

$$I_1 \cdot 5\Omega + (I_1 - I_2) \cdot 2\Omega + 3 \frac{V}{A} I_x = V_{s1}$$

On the right loop, we find

$$I_2 \cdot 3\Omega + (I_2 - I_1) \cdot 2\Omega = V_{s2} + 3 \frac{V}{A} I_x$$

we also know

$$I_2 = I_x$$

and therefore we find that

$$I_1 = \frac{1}{8\Omega} \cdot V_{s1} - \frac{1}{16\Omega} \cdot V_{s2}$$

$$I_2 = \frac{1}{8\Omega} \cdot V_{s1} + \frac{7}{16\Omega} \cdot V_{s2}$$

(b)

On the  $V_1$ , we find

$$V_1 = V_{s1}$$

and on the  $V_2$  (using KCL), we find

$$\frac{V_1 - V_2}{5\Omega} = \frac{V_2 - V_3}{2\Omega} + I_x$$

and on the  $V_3$ , we find that

$$V_3 = 3I_x$$

and on the  $V_4$ , we find that

$$V_4 = -V_{s2}$$




and we also know that

$$\frac{V_2 - V_4}{3\Omega} = I_x$$

therefore

$$\begin{aligned} V_1 &= V_{s_1} \\ V_2 &= \frac{3}{8}V_{s_1} + \frac{5}{16}V_{s_2} \\ V_3 &= \frac{3}{8}V_{s_1} + \frac{21}{16}V_{s_2} \\ V_4 &= -V_{s_2} \end{aligned}$$

(c)

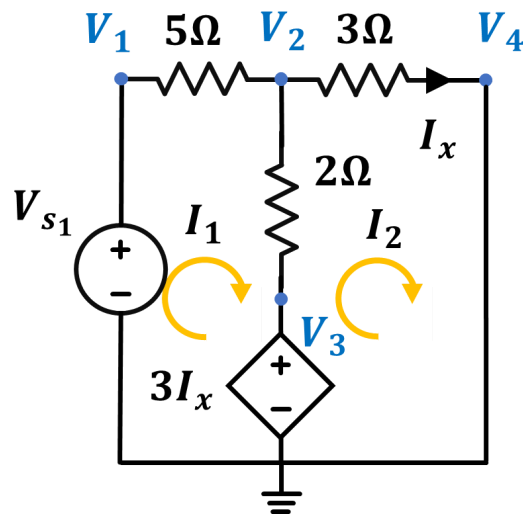

First remove  $V_{s_2}$ . Using node-voltage method, we see that

On the  $V_1$ , we find

$$V_1 = V_{s_1}$$

and on the  $V_2$  (using KCL), we find

$$\frac{V_1 - V_2}{5\Omega} = \frac{V_2 - V_3}{2\Omega} + I_x$$

and on the  $V_3$ , we find that

$$V_3 = 3\frac{\text{V}}{\text{A}}I_x$$

and on the  $V_4$ , we find that

$$V_4 = 0\text{V}$$

and we also know that

$$\frac{V_2 - V_4}{3\Omega} = \frac{V_2 - 0\text{V}}{3\Omega} = I_x$$

therefore

$$V_1 = V_{s_1}$$


$$V_2 = \frac{3}{8} V_{s_1}$$

$$V_3 = \frac{3}{8} V_{s_1}$$

$$V_4 = 0V$$

we find  $k_1 = \frac{3}{8}$

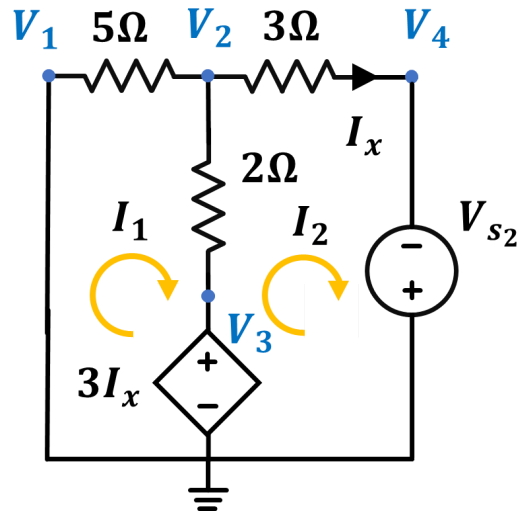Similarly, remove  $V_{s_1}$ . Using node-method again,



we find that

On the  $V_1$ , we find

$$V_1 = 0$$

and on the  $V_2$  (using KCL), we find

$$\frac{V_1 - V_2}{5\Omega} = \frac{V_2 - V_3}{2\Omega} + I_x$$

and on the  $V_3$ , we find that

$$V_3 = 3I_x$$

and on the  $V_4$ , we find that

$$V_4 = -V_{s_2}$$

and we also know that

$$\frac{V_2 - V_4}{3\Omega} = I_x$$

therefore

$$V_1 = 0V$$

$$V_2 = \frac{5}{16} V_{s_2}$$

$$V_3 = \frac{21}{16} V_{s_2}$$

$$V_4 = -V_{s_2}$$

we see that  $k_2 = \frac{21}{16}$ .

**(d)**

Set  $V_{s_1} = 10\text{V}$  and  $V_{s_2} = 4\text{V}$ .

$$I_1 = \frac{1}{8\Omega} \cdot 10\text{V} - \frac{1}{16\Omega} \cdot 4\text{V} = 1\text{A}$$

$$I_2 = \frac{1}{8\Omega} \cdot 10\text{V} + \frac{7}{16\Omega} \cdot 4\text{V} = 3\text{A}$$

**(e)**

Set  $V_{s_1} = 10\text{V}$  and  $V_{s_2} = 4\text{V}$ .

$$\begin{array}{l} V_1 = 10\text{V} \\ V_2 = \frac{3}{8} \cdot 10\text{V} + \frac{5}{16} 4\text{V} = 5\text{V} \\ V_3 = \frac{3}{8} \cdot 10\text{V} + \frac{21}{16} 4\text{V} = 9\text{V} \\ V_4 = -4\text{V} \end{array}$$