

### Question 1

$$R_{\text{opt}} = 45\Omega$$


### Question 2

$$R \geq 260.5\Omega \text{ or } R \leq 3.45\Omega$$

### Question 3

In this case, the combined effective resistance for these four resistor is still  $45\Omega$ , so the engine will still get  $120\text{mA}$  current supply. However, since these four resistor now in parallel, each of them will only receive  $120/4 = 30\text{mA}$  current now. The current is reduced to  $1/4$  of the original, while each resistors' resistance is increased by 4, this resulted in the power on each resistor reduced to  $1/4$  of the original ( $648\text{mW}/4 = 162\text{mW}$ ), which is in the limit of  $250\text{mW}$ .

### Question 4 & 5

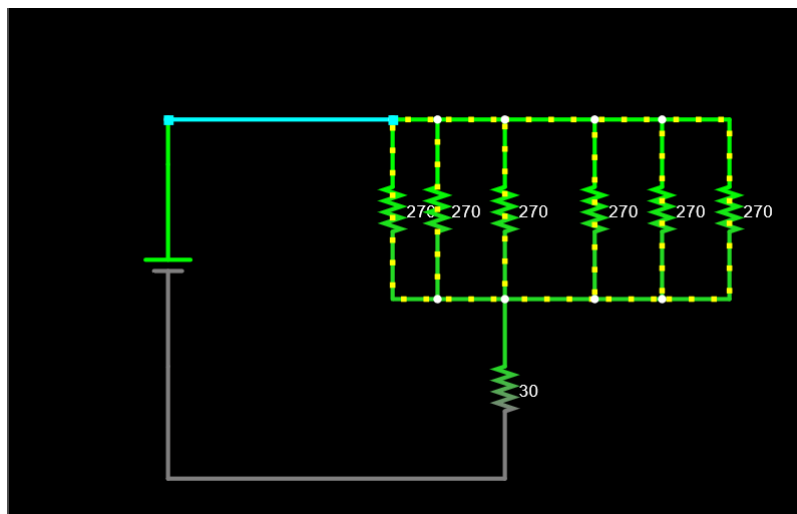

6 resistor of  $45 \cdot 6 = 270\Omega$  each in parallel also works.